

CSCE 5730/4730: Digital CMOS VLSI Design

Assignment # 4, Total Points = $2*50 = 100$.

Assigned Date: 20th Oct 2010 (Wed), Due Date: 27th Oct 2010 (Wed)

Instructor: Dr. Saraju P. Mohanty

1. Design a D Flip-Flop using 45nm technology in LTspice. Perform simulations to prove its functionality.
2. Briefly explain the concepts of: V_{Dsat} , I_{Dsat} , V_{th} , mobility, trans-conductance.